

PROIECT
LABORATOR
CIRCUITE INTEGRATE
DIGITALE



student: **ADRIAN ALEXANDRU BALUSĂ**

SERIA A

GRUPA 2123

îndrumător: **LAURA IOANA MIHĂILĂ**

CUPRINS


Cerințe + specificații proiect	pagina 3
Rezolvare pe hârtie	paginile 4 și 5
Sursă design + sursă simulare MUX 4:1	pag 6
Sursă design + sursă simulare BISTABIL D -	pag 7
Sursă design + sursă simulare INVERSOR -	pag 8
Sursă design + sursă simulare AUTOMAT ...	9-10

1. Rezolvarea corectă a temei de proiect pe hârtie
2. Circuitul combinational (Verificarea funcționalității circuitului)
3. Circuitul secvențial (Verificarea funcționalității circuitului)
4. Implementarea finală (Arhitectura se va descrie structural) (Verificarea funcționalității automatului)
5. Aspect documentație (foi de capăt, pagini numerotate etc.)

- I. Întrebările legate de proiect se pot pune numai la sfârșitul orei de laborator
- II. Simulările trebuie să scoată în evidență funcționalitatea circuitului conform tabelului de adevăr
- III. Documentația este un document PDF care va conține cerințele de mai sus, cât și rezolvarea pe hârtie a automatului, capturi de ecran la sursele de proiectare, sursele de simulare, rezultatele simulărilor și explicații
- IV. Se va realiza o arhivă cu proiectul final din Vivado
- V. Documentul PDF și arhiva cu proiectul final se vor trimite pe Teams profesorului de laborator până la data de 10.01.2023 ora 23:59 (Nerespectarea termenului limită duce la scăderea punctajului cu 2p)
- VI. Proiectul trebuie susținut personal, iar răspunsurile la întrebări vor influența nota finală

Recherche

→ automat de transitu:

 


→ Bistabil Δ (variante c)

n	clk	action
0	x	Reset
1	$\overline{\gamma}$	$Q^+ = D$
otherwise		Wait

→ MUX 4:1 et ports logice

Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+
0	0	0	1	1	0
0	0	1	1	0	0
0	1	0	x	x	x
0	1	1	1	0	1
1	0	0	0	0	0
1	0	1	1	1	1
1	1	0	0	1	1
1	1	1	0	0	1

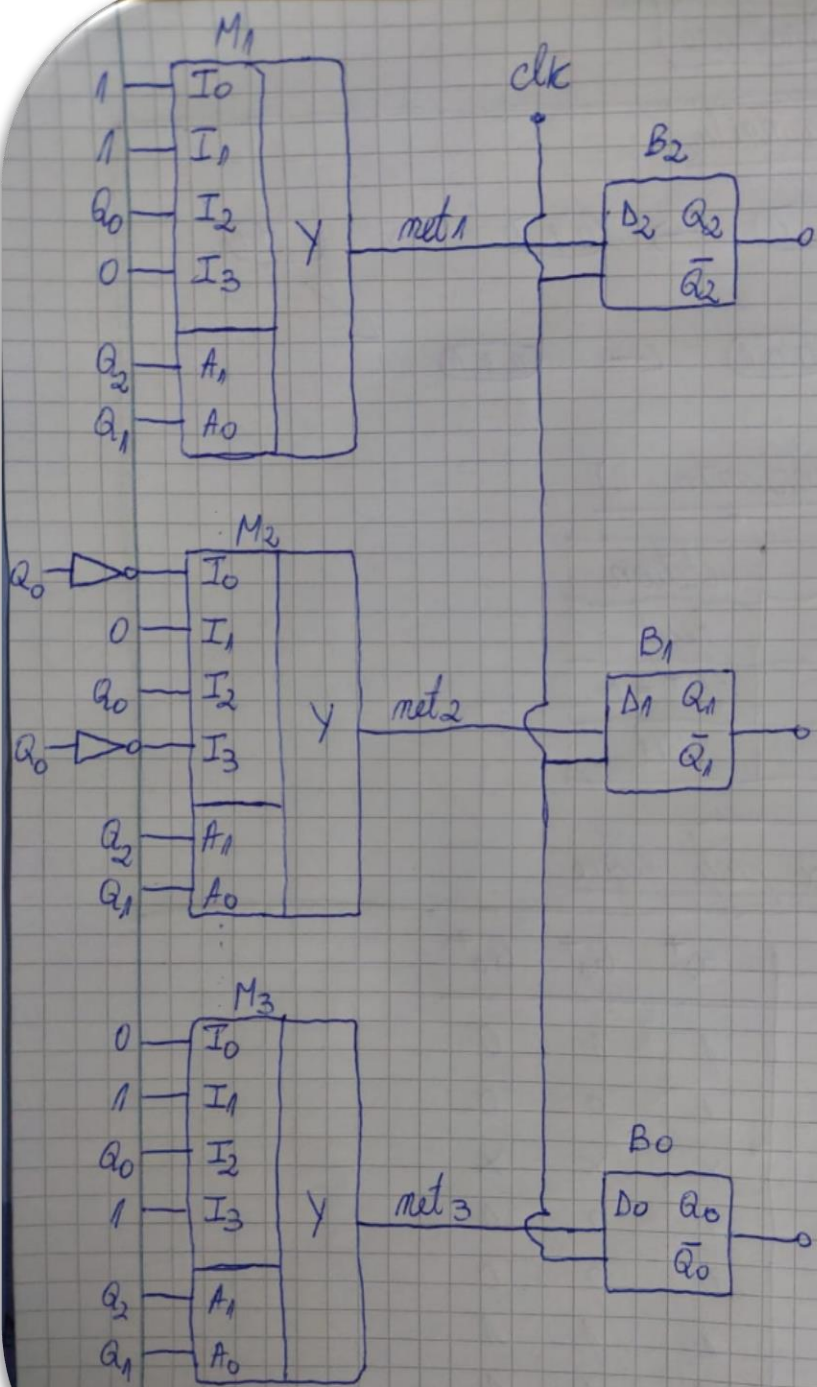

Sursa de design pentru Mux 4:1 si sursa de simulare a acestuia

```

entity mux4 is
    Port ( i0 : in STD_LOGIC;
           i1 : in STD_LOGIC;
           i2 : in STD_LOGIC;
           i3 : in STD_LOGIC;
           a2 : in STD_LOGIC;
           a1 : in STD_LOGIC;
           y : out STD_LOGIC);
end mux4;

architecture Behavioral of mux4 is

    signal adr : std_logic_vector(1 downto 0);

begin

    adr <= a2 & a1;

    with adr select
        y <= i0 when "00",
            i1 when "01",
            i2 when "10",
            i3 when "11",
            i0 when others;

end Behavioral;
    
```

```

entity m4_sim is
    -- Port ( );
end m4_sim;

architecture Behavioral of m4_sim is
    signal i0: std_logic;
    signal i1: std_logic;
    signal i2: std_logic;
    signal i3: std_logic;
    signal a2: std_logic;
    signal a1: std_logic;
    signal y: std_logic;

begin

    dut: entity work.mux4
        port map (
            i0 => i0,
            i1 => i1,
            i2 => i2,
            i3 => i3,
            a2 => a2,
            a1 => a1,
            y => y
        );
    
```

```

process
begin
    i0 <= '0';
    i1 <= '0';
    i2 <= '0';
    i3 <= '0';
    a2 <= '0';
    a1 <= '0';
    wait for 10 ns;

    i0 <= '1';
    i1 <= '0';
    i2 <= '0';
    i3 <= '1';
    a2 <= '0';
    a1 <= '1';
    wait for 10 ns;

    i0 <= '1';
    i1 <= '1';
    i2 <= '0';
    i3 <= '1';
    a2 <= '0';
    a1 <= '1';
    wait for 10 ns;


    i0 <= '1';
    i1 <= '1';
    i2 <= '1';
    i3 <= '0';
    a2 <= '1';
    a1 <= '0';
    wait for 10 ns;

    i0 <= '1';
    i1 <= '1';
    i2 <= '1';
    i3 <= '1';
    a2 <= '1';
    a1 <= '1';
    wait for 10 ns;

end process;
    
```

```

end Behavioral;
    
```

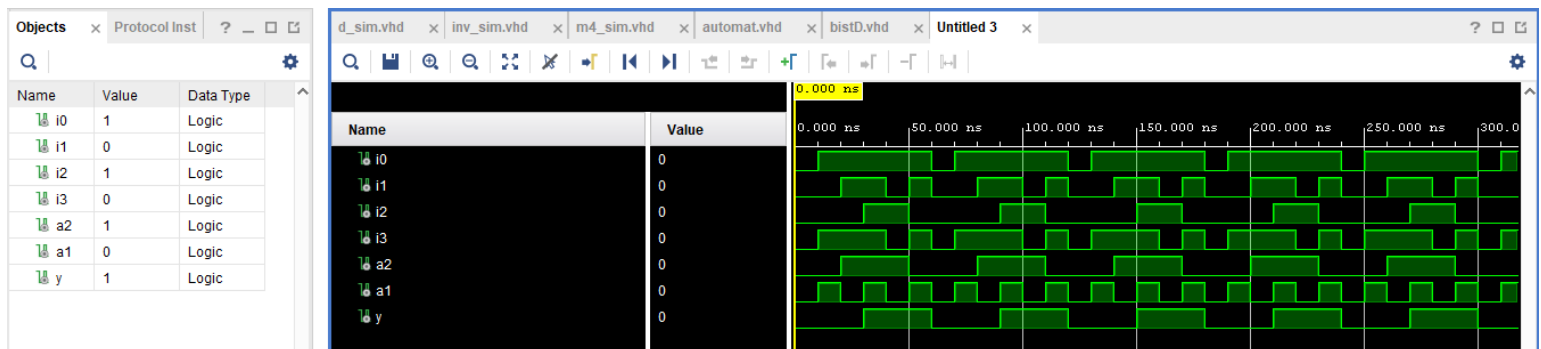

Sursa de design si sursa de simulare pentru bistabilul D

```
entity bistD is
  Port ( clk : in STD_LOGIC;
        d : in STD_LOGIC;
        r : in STD_LOGIC;
        q : out STD_LOGIC := '0';
        qneg : out STD_LOGIC := '1');
end bistD;

architecture Behavioral of bistD is
  signal qaux: std_logic;

begin

  q <= qaux;
  qneg <= not qaux;
  process(r, clk)
  begin
    if r = '0' then
      qaux <= '0';
    elsif falling_edge (clk) then
      qaux <= d;
    else
      qaux <= qaux;
    end if;
  end process;
end Behavioral;
```

```
entity d_sim is
  -- Port ( );
end d_sim;

architecture Behavioral of d_sim is
  signal d: std_logic;
  signal clk: std_logic;
  signal r: std_logic;
  signal q: std_logic;
  signal qneg: std_logic;


begin

  T: entity work.bistD port map (
    d => d,
    clk => clk,
    r => r,
    q => q,
    qneg => qneg
  );

  clk_gen: process
  begin
    clk <= '0';
    wait for 5 ns;
    clk <= '1';
    wait for 5 ns;
  end process;

  stim: process
  begin
    r <= '0';
    wait for 10 ns;
    r <= '1';
    wait for 10 ns;
    d <= '0';
    wait for 10 ns;
    d <= '1';
    wait for 10 ns;
  end process;
end Behavioral;
```

Name	Value	Data Type
d	0	Logic
clk	0	Logic
r	1	Logic
q	1	Logic
qneg	0	Logic

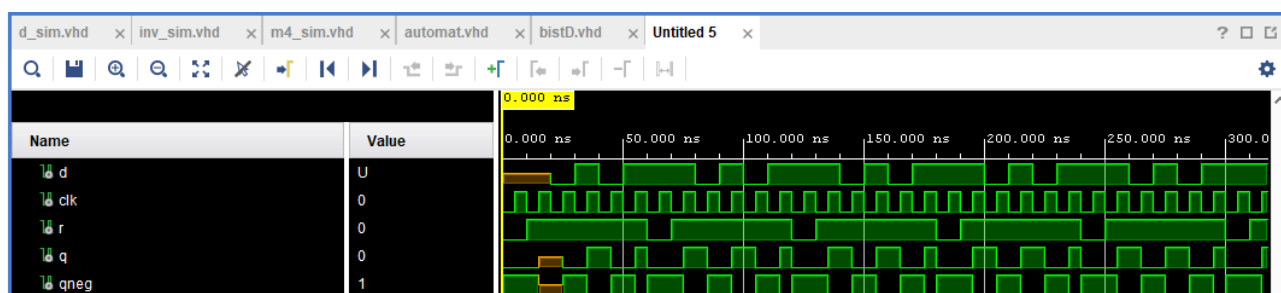

Sursa de design și sursa de simulare a inversorului

```
entity inversor is
    Port ( a : in STD_LOGIC;
          y : out STD_LOGIC);
end inversor;

architecture Behavioral of inversor is


begin

y <= not a;

end Behavioral;
```

```
entity inv_sim is
end inv_sim;

architecture Behavioral of inv_sim is
    signal a : std_logic;
    signal y : std_logic;
begin
    uut: entity work.inversor
        port map (
            a => a,
            y => y);
    stim_proc: process
    begin
        a <= '0';
        wait for 2 ns;
        a <= '1';
        wait for 2 ns;
        a <= '0';
        wait for 2 ns;
        a <= '1';
        wait for 2 ns;
        a <= '0';
        wait for 2 ns;
        a <= '1';
        wait for 2 ns;
        a <= '0';
        wait for 2 ns;
    end process;
end Behavioral;
```

 

Sursa de design pentru automat și sursa de simulare a acestuia

```
entity automat is
    Port ( clk : in STD_LOGIC;
          r : in STD_LOGIC;
          q : out STD_LOGIC_VECTOR (2 downto 0));
end automat;
```

```
architecture Behavioral of automat is
```

```
component mux4 is
    Port ( i0 : in STD_LOGIC;
          i1 : in STD_LOGIC;
          i2 : in STD_LOGIC;
          i3 : in STD_LOGIC;
          a1 : in STD_LOGIC;
          a2 : in STD_LOGIC;
          y : out STD_LOGIC);
end component mux4;
```

```
component bistD is
    Port ( clk : in STD_LOGIC;
          d : in STD_LOGIC;
          r : in STD_LOGIC;
          q : out STD_LOGIC;
          qneg : out STD_LOGIC);
end component bistD;
```

```
component inversor is
    Port ( a : in STD_LOGIC;
          y : out STD_LOGIC);
end component inversor;

signal net1, net2, net3, netA:std_logic;
signal qint:std_logic_vector(2 downto 0);
```

```
begin
```

```
q <= qint;
```

```
B2: bistD port map(clk => clk, d =>net1, r => r, q => qint(2));
B1: bistD port map(clk => clk, d =>net2, r => r, q => qint(1));
B0: bistD port map(clk => clk, d =>net3, r => r, q => qint(0));
```

```
M1: mux4 port map(i0=>'1', i1=>'1', i2=>qint(0), i3=>'0', a2=>qint(2), a1=>qint(1), y=>net1);
M2: mux4 port map(i0=>netA, i1=>'0', i2=>qint(0), i3=>netA, a2=>qint(2), a1=>qint(1), y=>net2);
M3: mux4 port map(i0=>'0', i1=>qint(0), i2=>qint(0), i3=>'1', a2=>qint(2), a1=>qint(1), y=>net3);
```

```
I1: inversor port map ( a => qint(0), y => netA);
```

```
end Behavioral;
```

```
entity test_automat is
-- Port ( );
end test_automat;

architecture Behavioral of test_automat is

    component automat is
        Port ( clk : in STD_LOGIC;
              r : in STD_LOGIC;
              q : out STD_LOGIC_VECTOR (2 downto 0));
    end component automat;

    signal clk, r:std_logic;
    signal q:std_logic_vector(2 downto 0);

begin

    UT:automat port map(clk, r, q);

    process
    begin
        clk<= '0'; wait for 1.2 ns;
        clk<= '1'; wait for 1.2 ns;

    end process;

    r <= '0' after 0 ns, '1' after 2.2 ns;

end Behavioral;
```

